

OPEN / CLOSED CIRCUITS - ACTIVITIES

<https://www.youtube.com/watch?v=-HpIzM11xJI>

- 1. When talking about batteries, what does the minus sign indicate ?**
- 2. What is a terminal?**
- 3. What does a circuit need to work?**
- 4. What is an open circuit? Do open circuits work?**
- 5. Do close circuits work?**